

# HW 3 - JA - Karnaugh Maps

|                |                             |
|----------------|-----------------------------|
| 👤 Owner        | 👤 John Akujobi              |
| 📌 Type         | Homework                    |
| 🕒 Created time | @September 5, 2023 10:06 PM |
| 📅 Due Date     | @September 13, 2023         |
| 🌟 Status       | In progress                 |

[homework3.docx](#)

[homework3.pdf](#)

## Q1

1. Calculate the minimal sum-of-products (SOP) and product-of-sums (POS) using Karnaugh Maps for the truth tables

Kmaps For No 1b HW3

|   |   | Bc |    |    |    |
|---|---|----|----|----|----|
|   |   | 00 | 01 | 11 | 10 |
| A | 0 | 0  | 1  | 0  | 0  |
|   | 1 | 0  | 0  | 1  | 1  |

Kmaps For No 1a HW3

|   |   | B |   |
|---|---|---|---|
|   |   | 0 | 1 |
| A | 0 | 0 | 1 |
|   | 1 | 1 | 1 |

Q1 A

1.

| A | B | Y |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

## POS

- $Y = A+B$
- Cost = 3

## SOP

- $Y = A + B$

## Q1 B

| A | B | C | Y |           |
|---|---|---|---|-----------|
| 0 | 0 | 0 | 0 |           |
| 0 | 0 | 1 | 1 | $A'.B'.C$ |
| 0 | 1 | 0 | 0 |           |
| 0 | 1 | 1 | 0 |           |
| 1 | 0 | 0 | 0 |           |
| 1 | 0 | 1 | 0 |           |
| 1 | 1 | 0 | 1 | $A.B.C'$  |
| 1 | 1 | 1 | 1 | $A.B.C$   |

## SOP:


- $Y = A.B + (A'.B'.C)$
- Cost = 11

## POS:

- $Y = (B+C).(A+C).(A+B').(A'+B)$

- Cost = 17

Karnaugh Maps HW 1b.cv

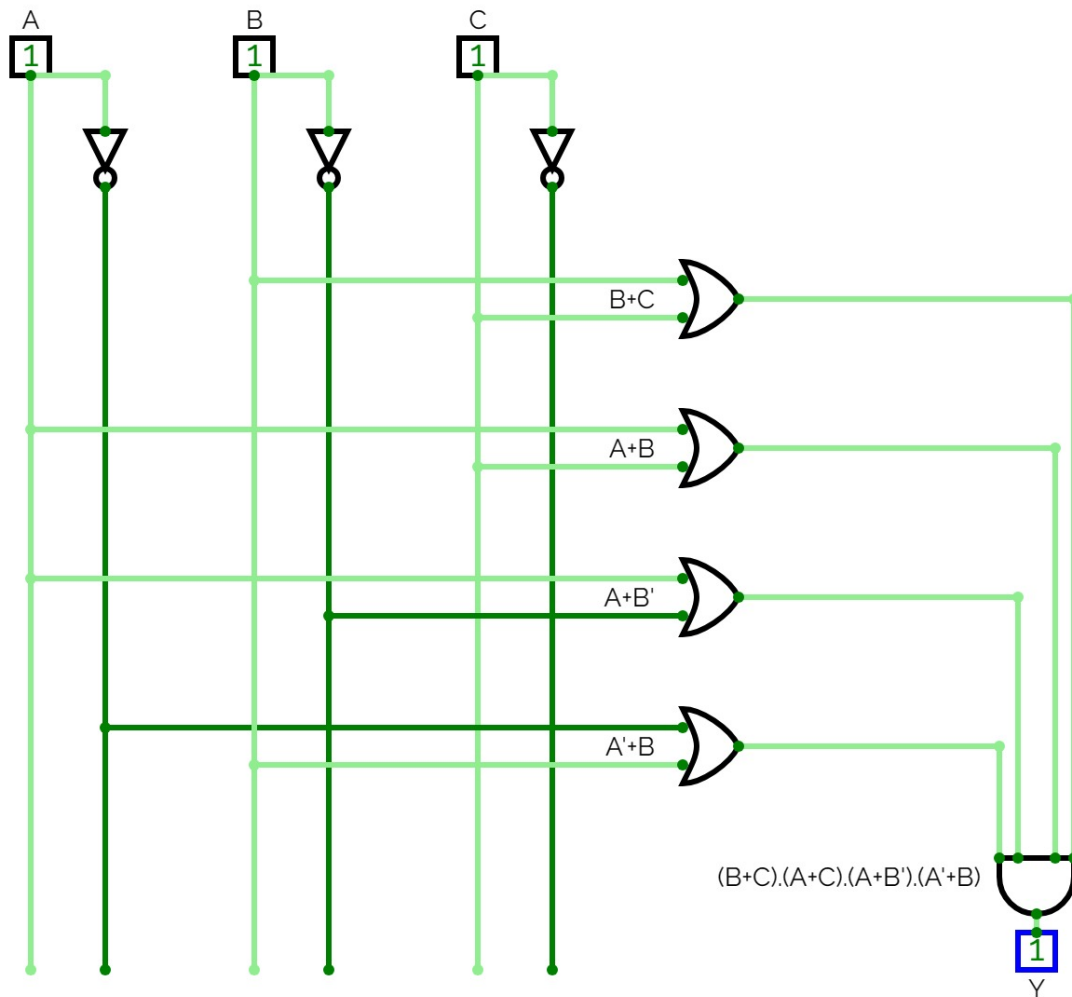

POS Circuit

c. What is the cost of the two circuits? State which is cheaper, SOP or POS.

Q1a

- SOP = 3

- POS = 3
- They were the same

Q1b

- SOP =
- POS =
- was cheaper tha

## Q 2


- Find minimal Boolean equations for the truth table below using both SOP and POS forms using K-maps.

| A | B | C | D | Y |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | X |
| 0 | 0 | 0 | 1 | X |
| 0 | 0 | 1 | 0 | X |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | X |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | X |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | X |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | X |

| A | B | C | D | Y |
|---|---|---|---|---|
| 1 | 1 | 1 | 1 | 1 |

## K-Maps




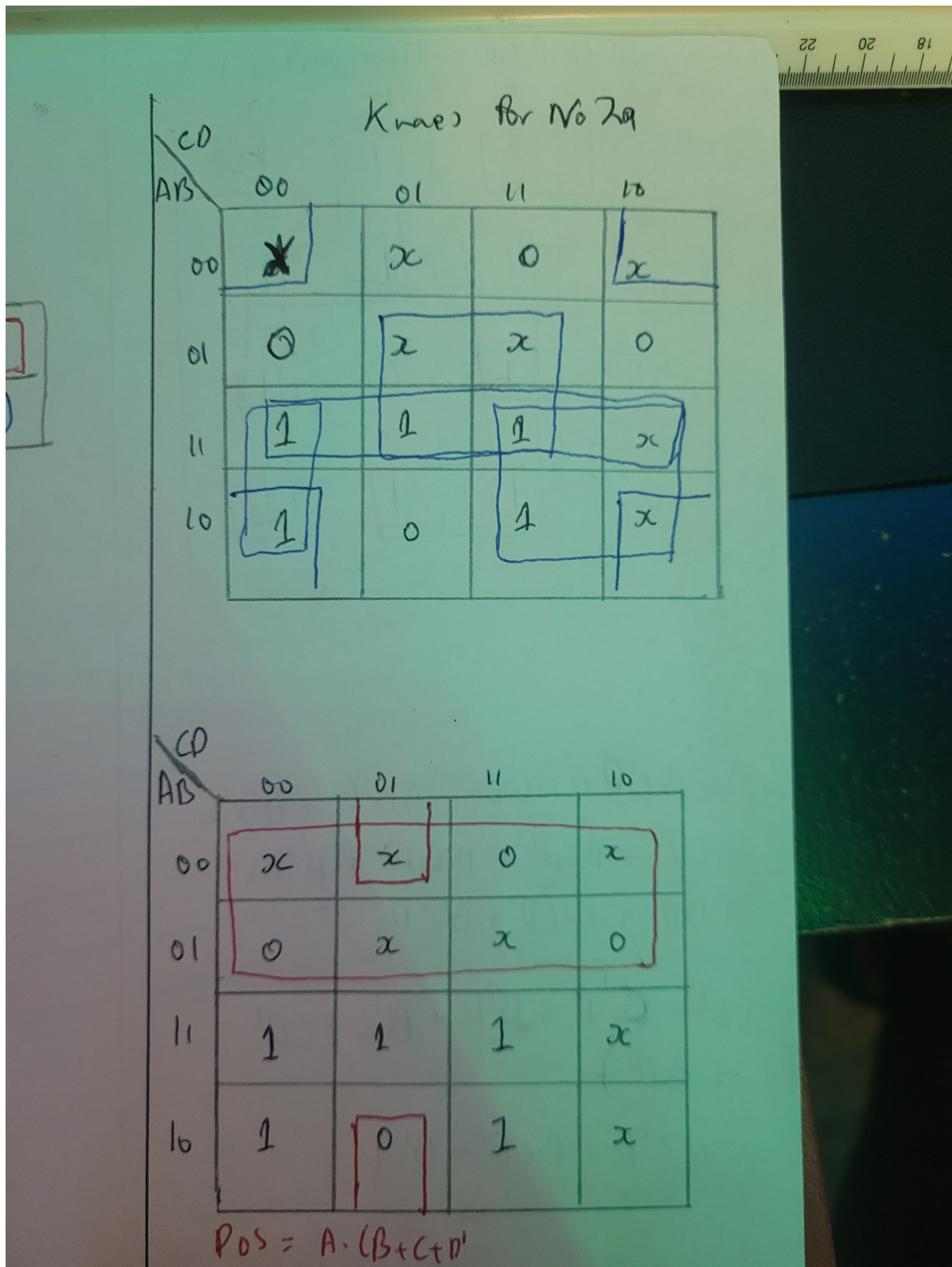

SOP

- $Y = AB + AC + AD' + BD + B'D'$
- $Y = AB + AC + AD' + \cancel{BD + B'D'}$
- $Y = A.B + A.C + A.D'$
- Cost = 14

SOP Q2-1 HW3.cv

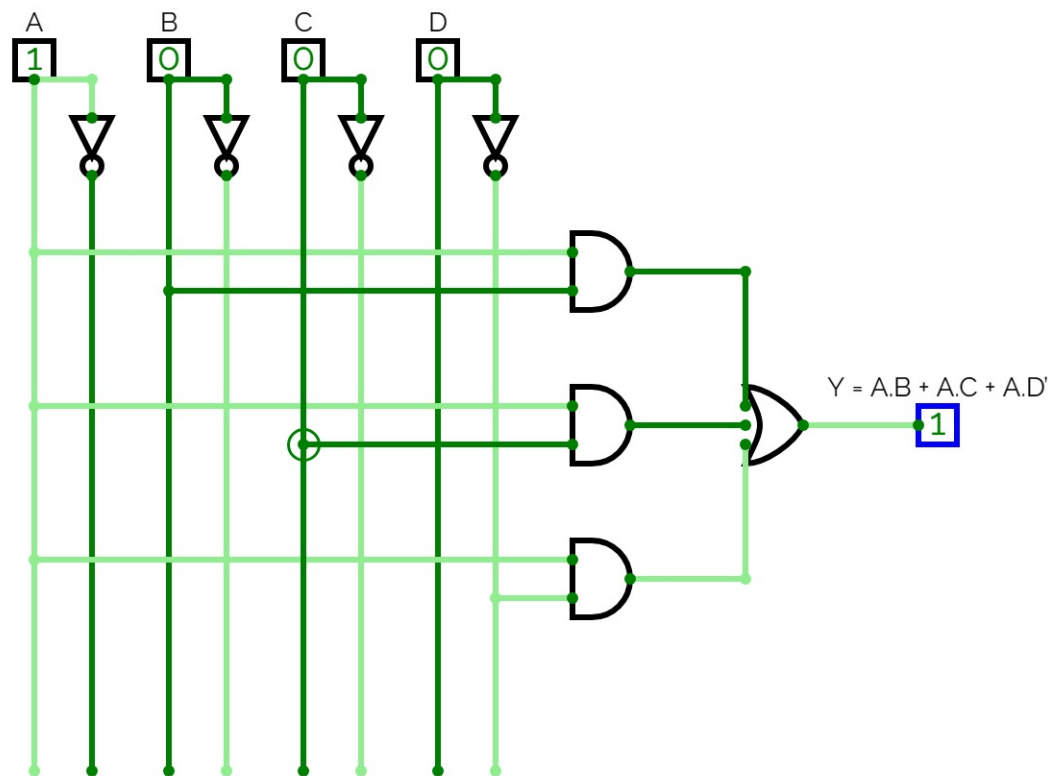


## POS

- $Y = A.(B+C+D')$



POS Q2-1 HW3.cv

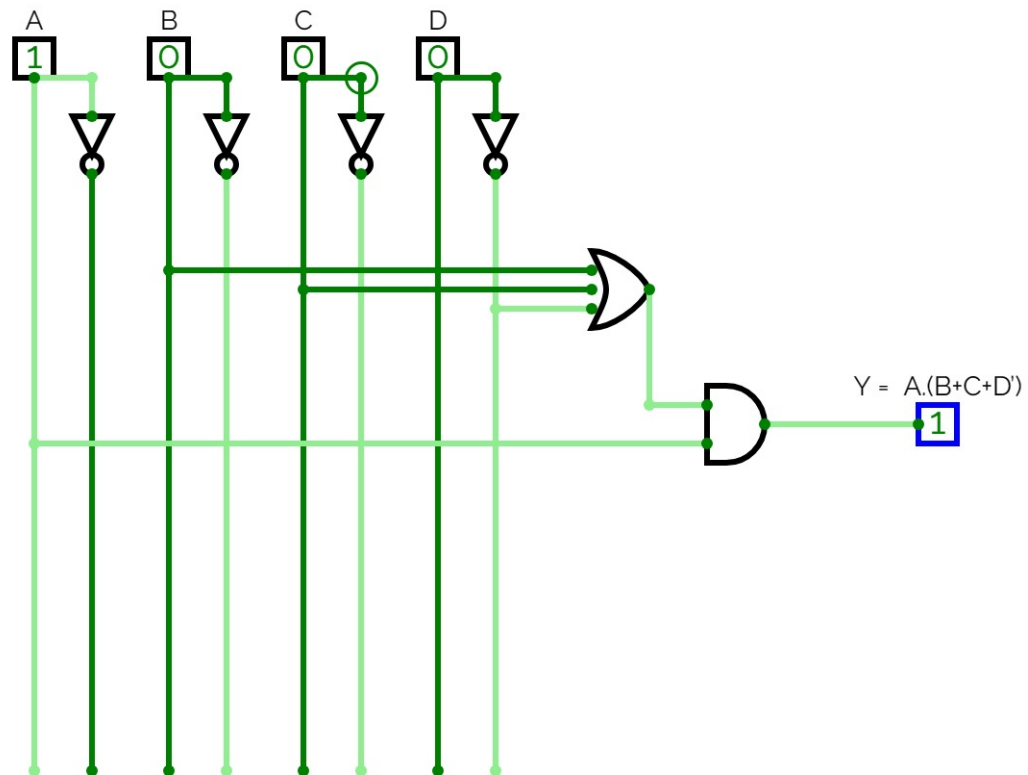


1. Determine which circuit is cheaper

- The POS circuit is cheaper

2. Draw the circuit for the **cheapest implementation** using only NAND gates (if sum-of-products form) or NOR gates (if product-of-sums form). You may also use inverters if needed.

NAND Gates of Q2A HW 3.cv

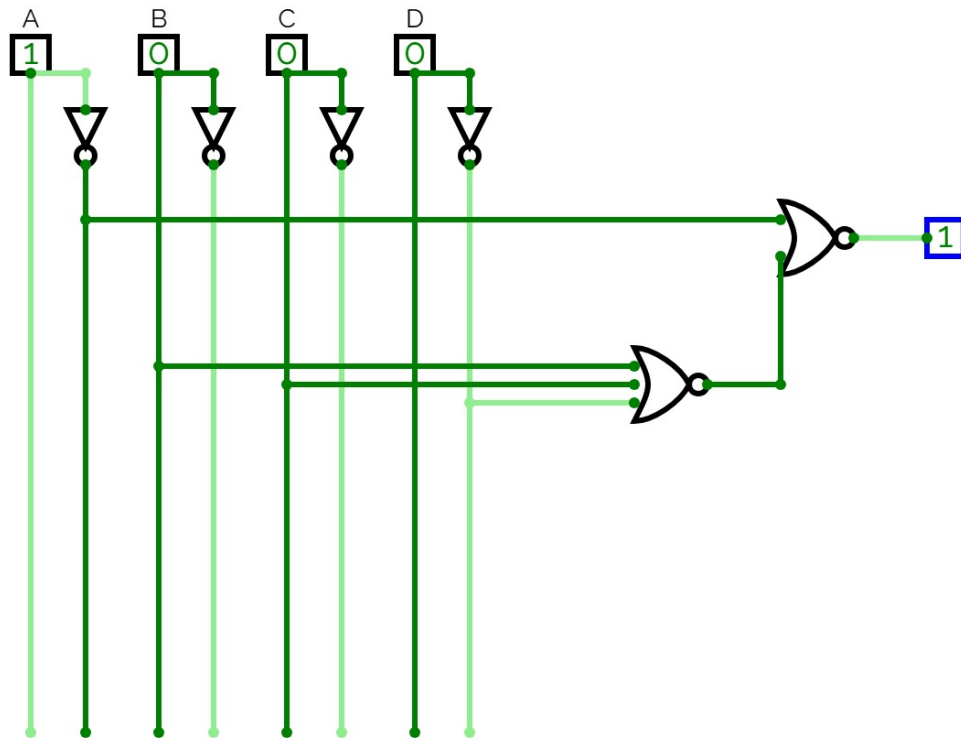

Using NOR gates

### Q3

Calculate the minimal SOP and POS for the following function using K-maps:

1. Write two sentences on your solution to SOP; is it unique?

$$F(A,B,C,D) = \prod (0,1,2,4,8,15)$$

**POS:**

- $(A+B+C) \cdot (A+B+D) \cdot (A+C+D) \cdot (B+C+D) \cdot (A'+B'+C'+D')$

**SOP:**

- $AC' + BC'D + AC'D + AB'D + AB'C + ACD' + BCD' + ABD' + A'BC + A'BD + A'CD + B'CD$
- It looks like it can be simplified by bring groups together, but after trying multiple times, it looked like it could not be simplified more.

- Each of the groups had only one input that was inverted. Eg C in BC'D

